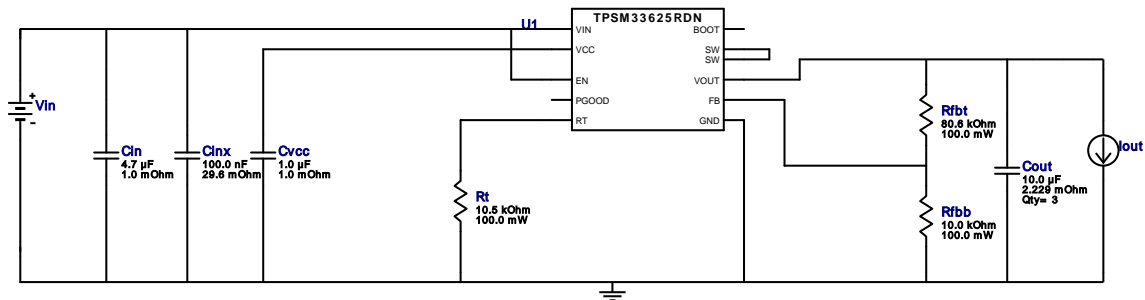








## WEBENCH® Design Report







Design : 3 TPSM33625RDNR  
TPSM33625RDNR 10V-36V to 9.00V @ 1.5A










## Electrical BOM

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cin	MuRata	GRM32ER71H475KA88L Series= X7R	Cap= 4.7 uF ESR= 1.0 mOhm VDC= 50.0 V IRMS= 6.0 A	1	\$0.16	 1210 15 mm <sup>2</sup>
Cinx	TDK	CGA3E2X7R1H104K080AA Series= X7R	Cap= 100.0 nF ESR= 29.6 mOhm VDC= 50.0 V IRMS= 971.99 mA	1	\$0.01	 0603 5 mm <sup>2</sup>
Cout	TDK	C3216X7R1V106K160AC Series= X7R	Cap= 10.0 uF ESR= 2.229 mOhm VDC= 35.0 V IRMS= 4.8593 A	3	\$0.18	 1206_180 11 mm <sup>2</sup>
Cvcc	Taiyo Yuden	EMK107B7105KA-T Series= X7R	Cap= 1.0 uF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0603 5 mm <sup>2</sup>
Rfbb	Yageo	RC0603FR-0710KL Series= ?	Res= 10.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm <sup>2</sup>
Rfbt	Vishay-Dale	CRCW060380K6FKEA Series= CRCW..e3	Res= 80.6 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm <sup>2</sup>
Rt	Vishay-Dale	CRCW060310K5FKEA Series= CRCW..e3	Res= 10.5 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm <sup>2</sup>
U1	Texas Instruments	TPSM33625RDNR	Switcher	1	\$1.40	RPE0009A 9 mm <sup>2</sup>

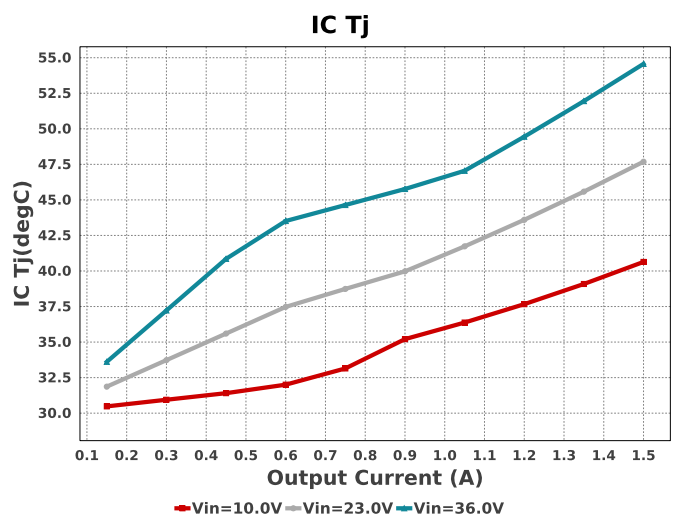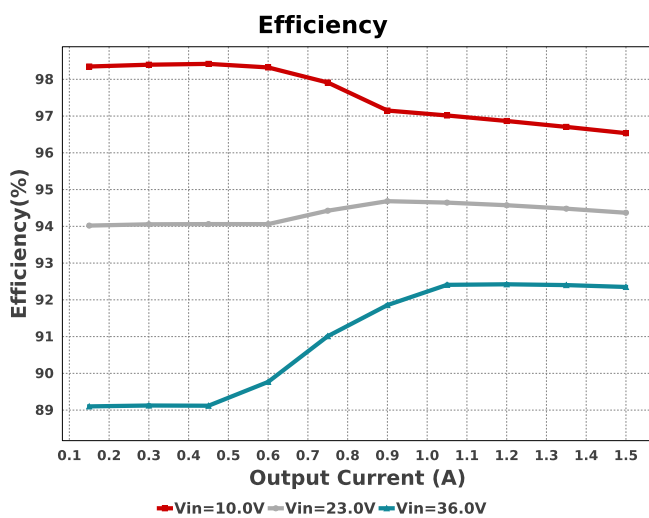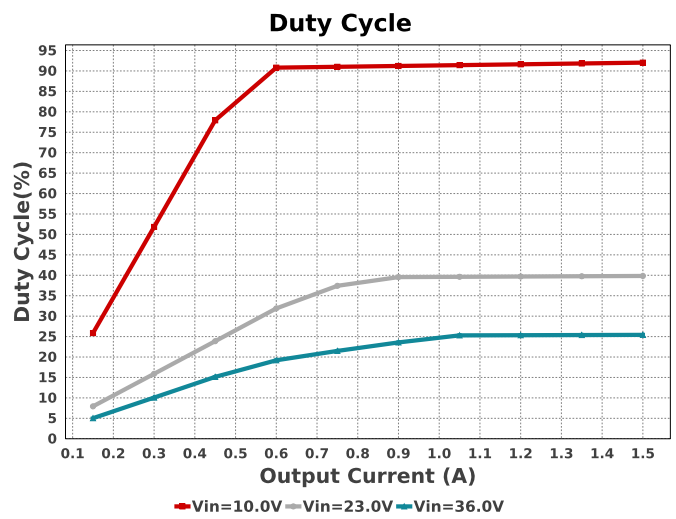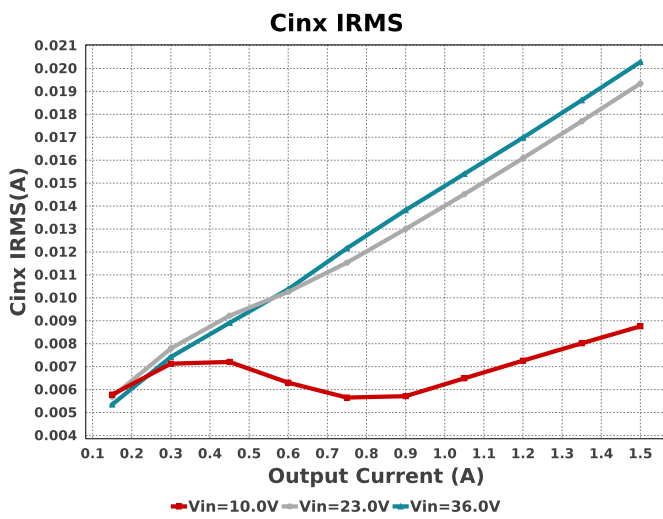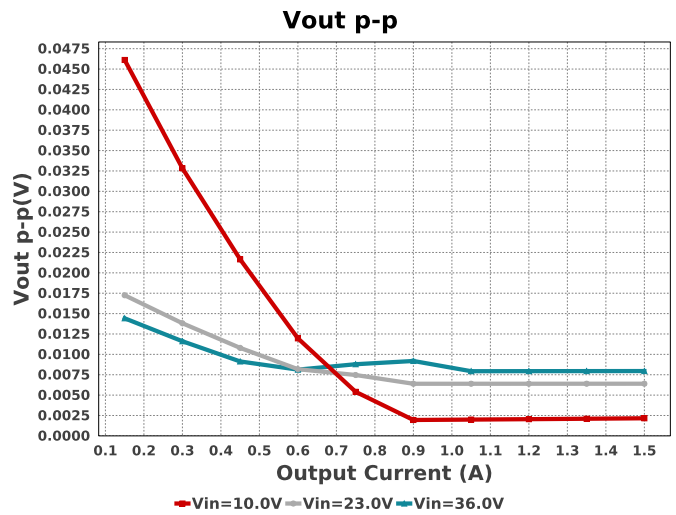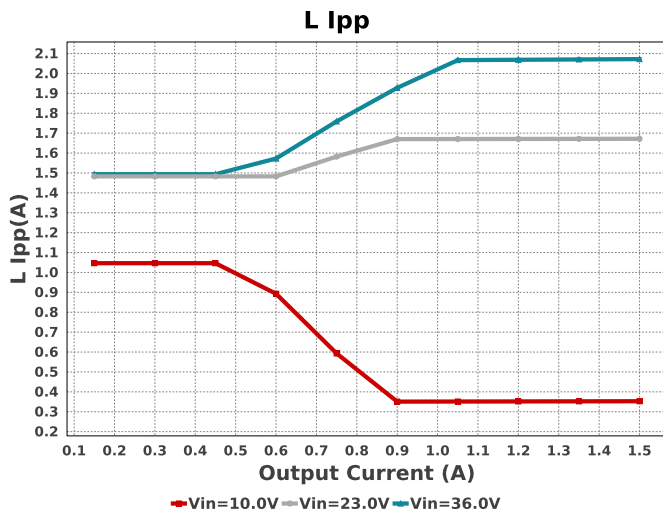

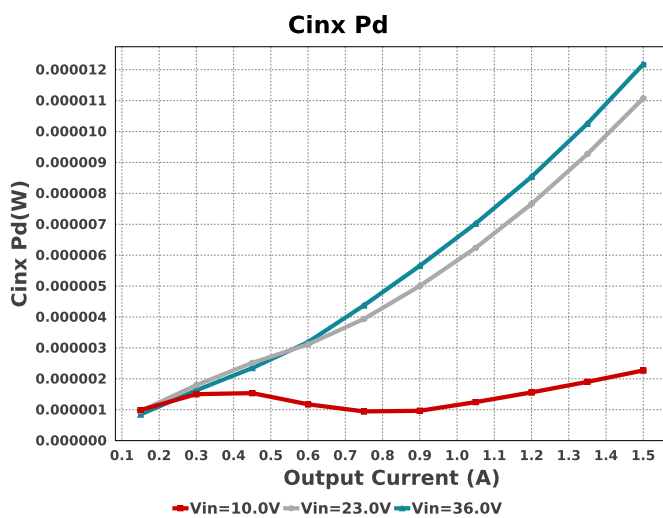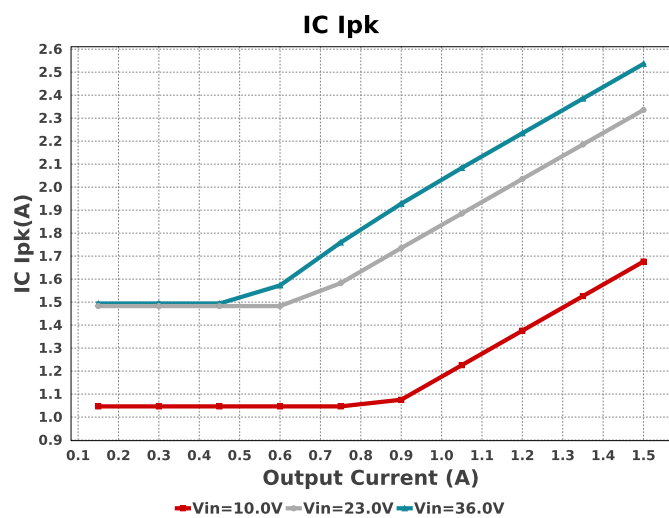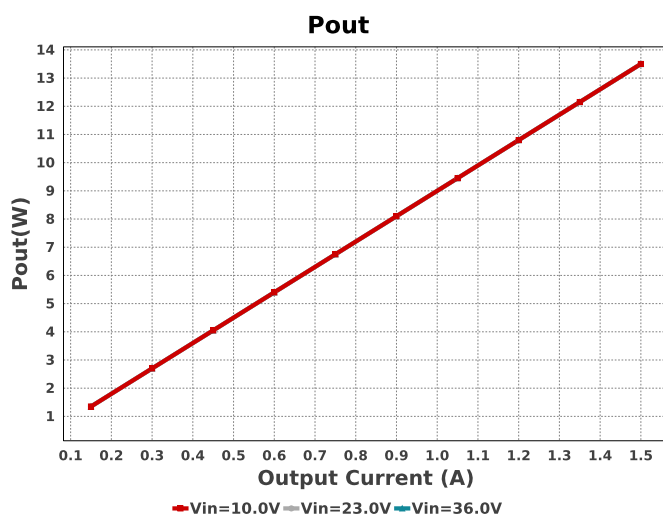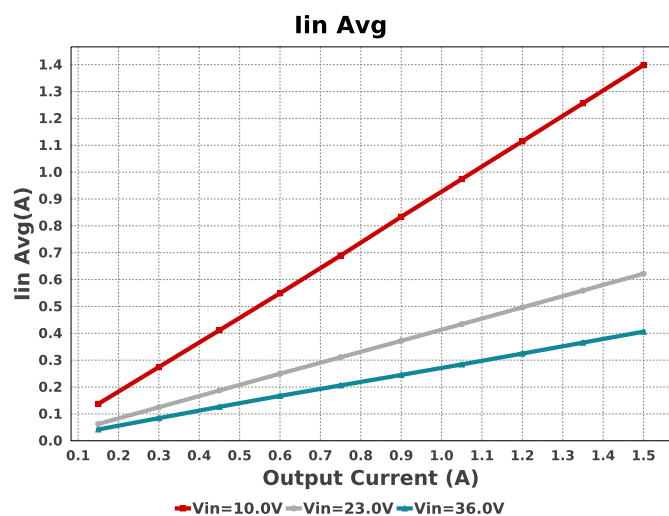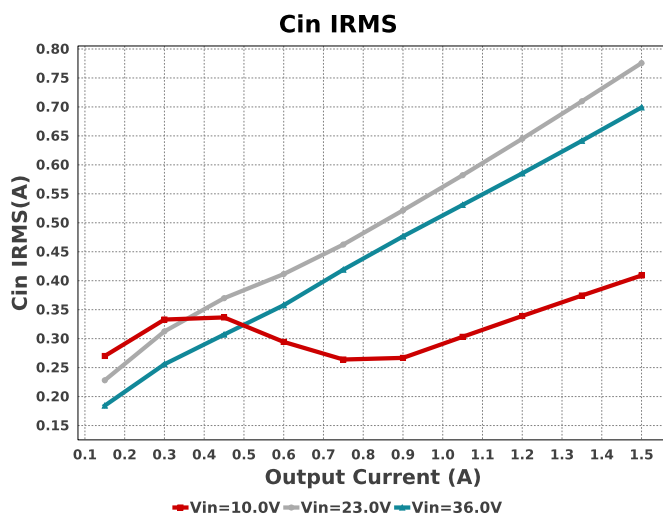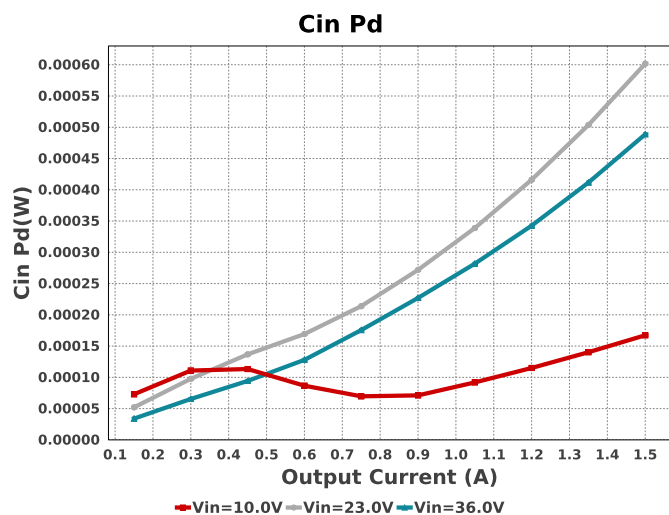

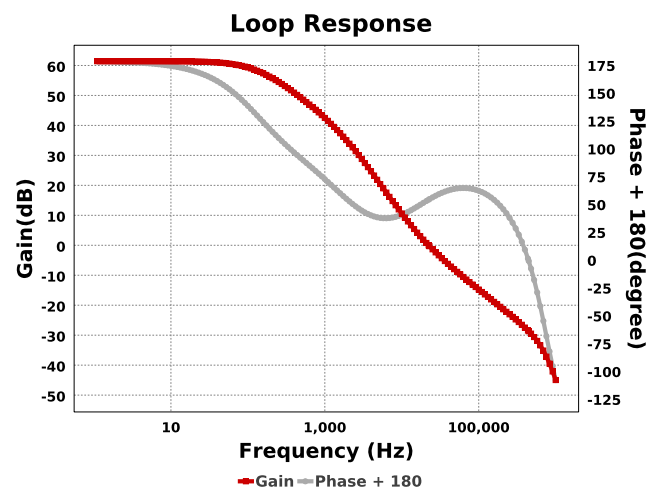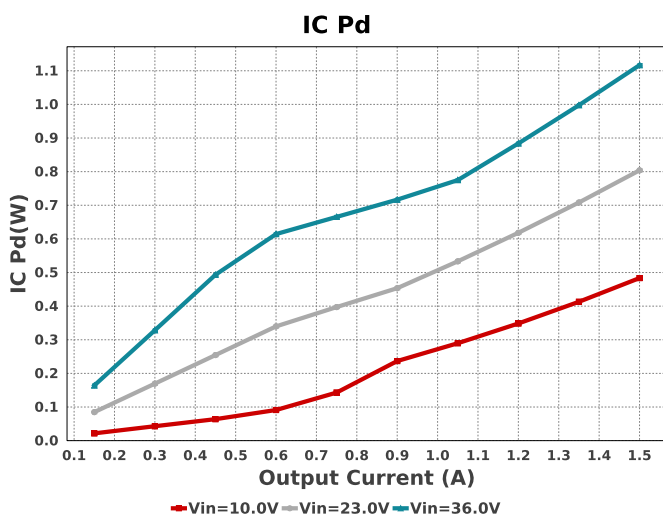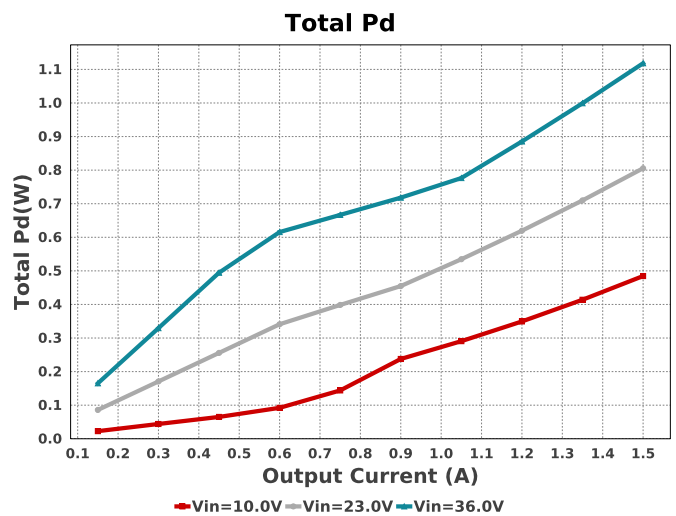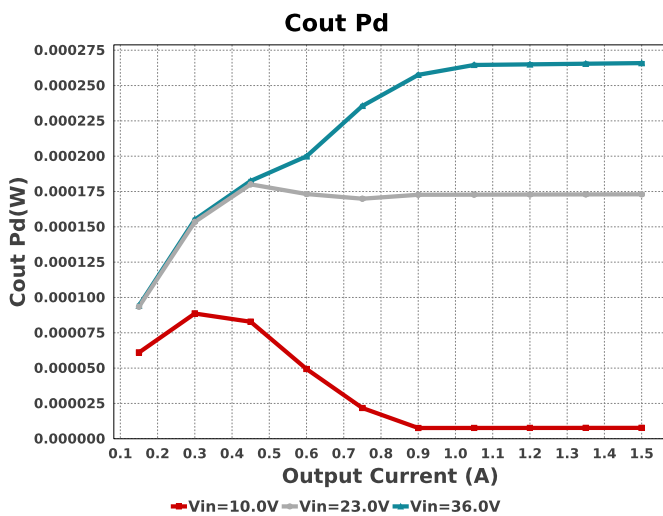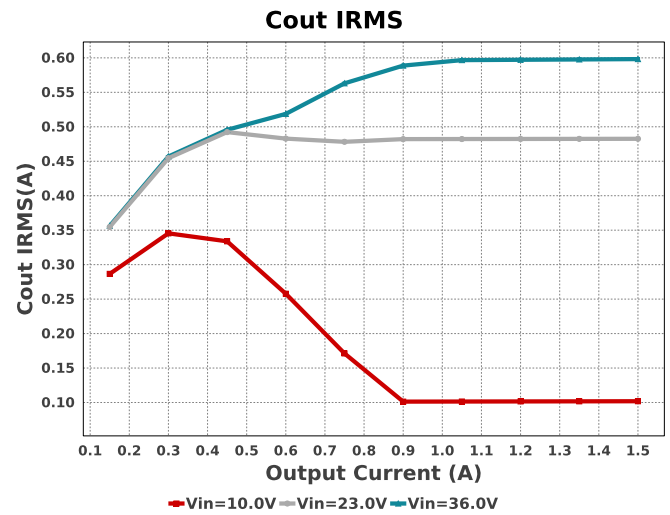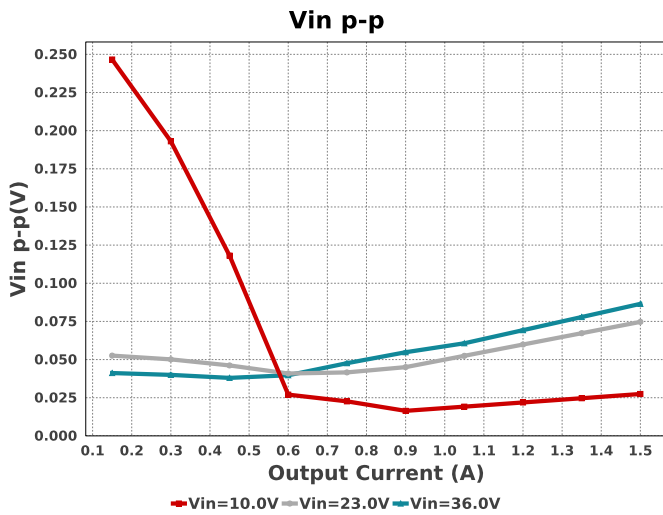

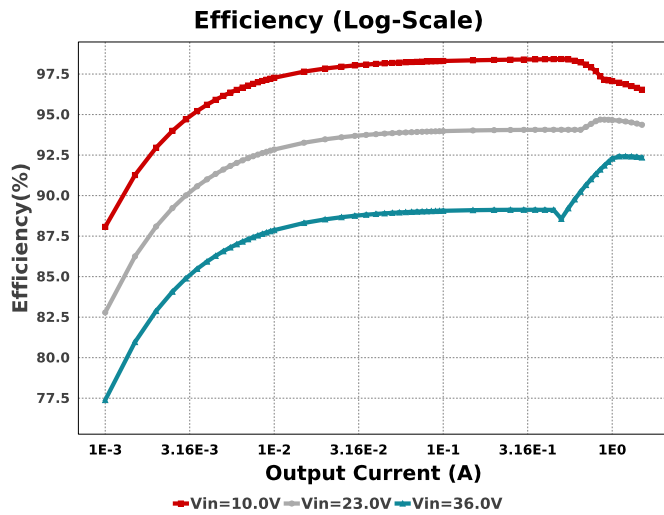

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	699.093 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	488.73 $\mu$ W	Capacitor	Input capacitor power dissipation
3.	Cinx IRMS	20.283 mA	Capacitor	Bulk capacitor RMS ripple current
4.	Cinx Pd	12.177 $\mu$ W	Capacitor	Bulk capacitor power dissipation
5.	Cout IRMS	598.199 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	265.88 $\mu$ W	Capacitor	Output capacitor power dissipation
7.	IC Ipk	2.536 A	IC	Peak switch current in IC
8.	IC Pd	1.117 W	IC	IC power dissipation
9.	IC Tj	54.567 degC	IC	IC junction temperature
10.	IC Tolerance	12.5 mV	IC	IC Feedback Tolerance
11.	ICThetaJA Effective	22.0 degC/W	IC	Effective IC Junction-to-Ambient Thermal Resistance
12.	Iin Avg	406.07 mA	IC	Average input current
13.	Cin Pd	488.73 $\mu$ W	Power	Input capacitor power dissipation
14.	Cinx Pd	12.177 $\mu$ W	Power	Bulk capacitor power dissipation
15.	Cout Pd	265.88 $\mu$ W	Power	Output capacitor power dissipation
16.	IC Pd	1.117 W	Power	IC power dissipation
17.	Total Pd	1.118 W	Power	Total Power Dissipation
18.	BOM Count	10	System	Total Design BOM count
19.	Cross Freq	22.343 kHz	Information	Bode plot crossover frequency
20.	Duty Cycle	25.419 %	System	Duty cycle
21.	Efficiency	92.35 %	Information	Steady state efficiency
22.	FootPrint	80.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
23.	Frequency	1.494 MHz	Information	Switching frequency
24.	Gain Marg	-28.679 dB	System	Bode Plot Gain Margin
25.	Iout	1.5 A	Information	Iout operating point
26.	L Ipp	2.072 A	System	Peak-to-peak inductor ripple current
27.	Low Freq Gain	61.427 dB	Information	Gain at 1Hz
28.	Mode	CCM	System	Conduction Mode
29.	Phase Marg	55.106 deg	Information	Bode Plot Phase Margin
30.	Pout	13.5 W	System	Total output power
31.	Total BOM	\$2.15	Information	Total BOM Cost
32.	Vin	36.0 V	System	Vin operating point
33.	Vin p-p	86.501 mV	Information	Peak-to-peak input voltage
34.	Vout	9.0 V	System	Operational Output Voltage

#	Name	Value	Category	Description
35.	Vout Actual	9.06 V	System Information	Vout Actual calculated based on selected voltage divider resistors
36.	Vout Tolerance	3.07 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
37.	Vout p-p	7.953 mV	System Information	Peak-to-peak output ripple voltage

## Design Inputs

Name	Value	Description
Iout	1.5	Maximum Output Current
VinMax	36.0	Maximum input voltage
VinMin	10.0	Minimum input voltage
Vout	9.0	Output Voltage
base_pn	TPSM33625	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature
UserFsw	1000.0 k	Customer Selected Frequency

## WEBENCH® Assembly

### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of  $C_{in}$  and  $C_{out}$ , and the inductance and DC resistance of  $L1$  before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

### Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 10.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to  $V_{in}$  and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from  $V_{out}$  and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between  $V_{in}$  and GND, a load is connected between  $V_{out}$  and GND and a current meter is connected in series between  $V_{out}$  and the load. The load must be able to handle at least rated output power + 50% ( 7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



### Design Assistance

1. Master key : 2703625DAEF3863DD9FE52FC7C08223E[v1]
2. **TPSM33625** Product Folder : <http://www.ti.com/product/TPSM33625> : contains the data sheet and other resources.

**Important Notice and Disclaimer**

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with TI products.